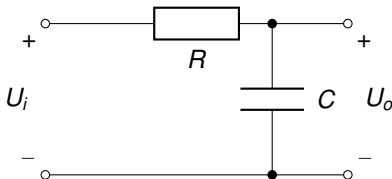


Embedded Systems Hands-On 1: Design and Implementation of Hardware/Software Systems

Electrical Engineering Brief



TECHNISCHE
UNIVERSITÄT
DARMSTADT





- ▶ Basic terms of electrostatics
- ▶ Passive components in electronic circuits
- ▶ Semiconductors


Electric Charge



TECHNISCHE
UNIVERSITÄT
DARMSTADT

- ▶ Q [As] or [Coulomb]
- ▶ Multiple of elementary charge $Q = z \cdot e_0, z \in \mathbb{Z}, e_0 = 1.6 \cdot 10^{-19} \text{As}$


$$F \propto \frac{Q_1 Q_2}{r^2}$$

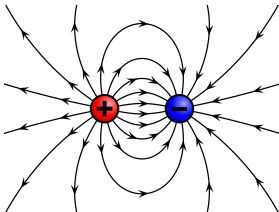

- ▶ Force per Charge

$$E = \frac{F_C}{q}, \left[\frac{V}{m} \right]$$

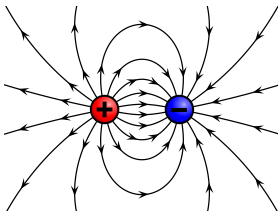- ▶ Vectorial field quantity
- ▶ Visualized by field lines
 - ▶ Positive to negative
 - ▶ Orthogonal to surface
 - ▶ Density \propto intensity



Electric Potential




TECHNISCHE
UNIVERSITÄT
DARMSTADT

- Specific energy required to move the test charge *into* electric field

$$\varphi = \frac{W}{Q}, [V]$$

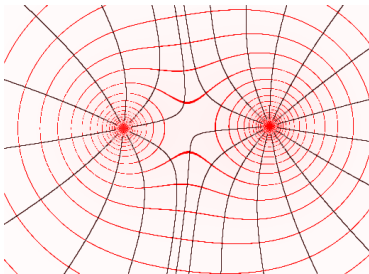- Scalar field quantity
- Visualized by lines of equal potential





- ▶ Specific energy required to move the test charge *inside* the electric field

$$U = \Delta\varphi, [V]$$

- ▶ Difference in potentials

Electric Capacity



TECHNISCHE
UNIVERSITÄT
DARMSTADT

$$C = \frac{Q}{U}, \left[\frac{As}{V} \right], [F]$$

- ▶ Parallel-plate capacitor



$$C \propto \frac{A}{d}$$

- ▶ Parallel circuit

$$C = C_1 + C_2$$

- ▶ Series circuit

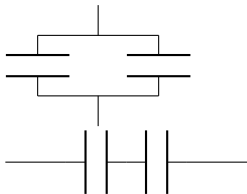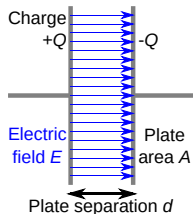
$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Leftrightarrow C = \frac{C_1 C_2}{C_1 + C_2}$$



- ▶ Flow of electric charge through a region

$$I = \frac{\Delta Q}{\Delta t}, [A]$$

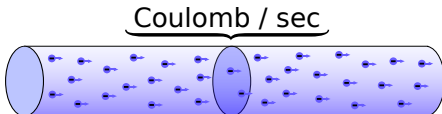- ▶ Current flow: $+$ \rightarrow $-$
- ▶ Electron movement: $-$ \rightarrow $+$



- ▶ Ohm's law

$$R = \frac{U}{I}$$

- ▶ Conductor type


- ▶ Metallic $R \propto \sigma l A^{-1}$
- ▶ Isolator $R \rightarrow \infty$
- ▶ Semiconductor *non-linear*

- ▶ Series circuit

$$R = R_1 + R_2$$

- ▶ Parallel circuit
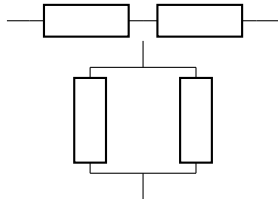
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \Leftrightarrow R = \frac{R_1 R_2}{R_1 + R_2}$$





- ▶ Work done per unit time

$$P = \frac{UQ}{t} = UI$$

- ▶ For resistive loads


$$P = I^2 R = \frac{U^2}{R}$$

Kirchhoff's circuit laws



TECHNISCHE
UNIVERSITÄT
DARMSTADT


- ▶ Junction rule (charge conservation)

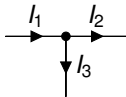

$$\sum_k I_k = 0$$


Kirchhoff's circuit laws

- ▶ Junction rule (charge conservation)

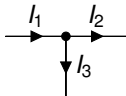

$$\sum_k I_k = 0$$

- ▶ Mesh rule (potential conservation)

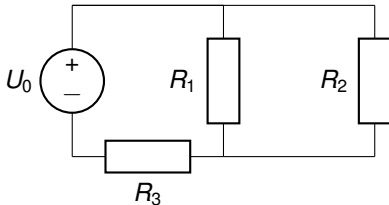

$$\sum_k U_k = 0$$

- ▶ Mesh 1: $U_0 = U_{R1} + U_{R2}$
- ▶ Mesh 2: $U_{R1} = U_{R2}$
- ▶ Mesh 3: $U_0 = U_{R2} + U_{R3}$

Voltage divider




TECHNISCHE
UNIVERSITÄT
DARMSTADT

- ▶ Junction rule $I = I_{R_1} = I_{R_2}$
- ▶ Ohm's Law $U_{R_x} = R_x \cdot I_{R_x}$
- ▶ Series circuit $U = (R_1 + R_2) \cdot I$
- ▶ Mesh rule $U = U_{R_1} + U_{R_2}$

- ▶ Divider relation

$$U_{R_x} = U \frac{R_x}{R_1 + R_2}$$


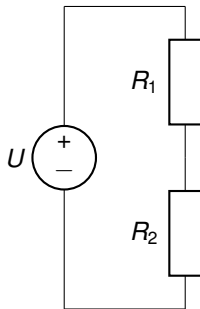


Electrical sources



TECHNISCHE
UNIVERSITÄT
DARMSTADT

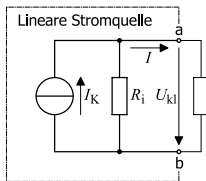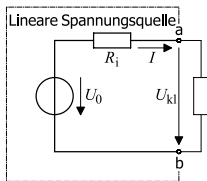- ▶ Voltage source
 - ▶ Constant voltage, independent of current
- ▶ Current source
 - ▶ Constant current, independent of voltage
- ▶ Real world
 - ▶ Linear power supply (due to internal resistance)
 - ▶ Switched-mode power supply
- ▶ Bench power supply
 - ▶ Set voltage, limit current to avoid damage



Charging a Capacitor



TECHNISCHE
UNIVERSITÄT
DARMSTADT

- ▶ Mesh rule
- ▶ Capacitor
- ▶ Ohm's law
- ▶ Current flow
- ▶ Substitute
- ▶ Differential equation
- ▶ Charge voltage
- ▶ Charge current

$$U_0 = U_R(t) + U_C(t)$$

$$U_C(t) = \frac{1}{C} Q(t)$$

$$U_R(t) = R I(t)$$



$$I(t) = \frac{\Delta Q(t)}{\Delta t}$$

$$\frac{U_0}{R} = \frac{\Delta Q(t)}{\Delta t} + \frac{Q(t)}{RC}$$

...

$$U_C(t) = U_0 \left(1 - e^{-\frac{t}{RC}} \right)$$
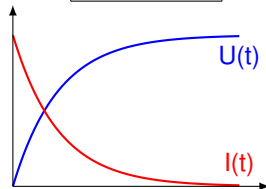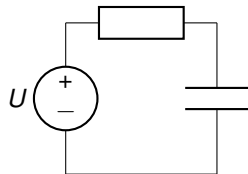
$$I_C(t) = \frac{U_0}{R} e^{-\frac{t}{RC}}$$



- ▶ Complex quantity

$$Z = R + jX$$

- ▶ Angular frequency $\omega = 2\pi f$


- ▶ Capacitor

$$Z_C = \frac{1}{j\omega C}$$


- ▶ Inductor

$$Z_L = j\omega L$$

► Example: First order low-pass

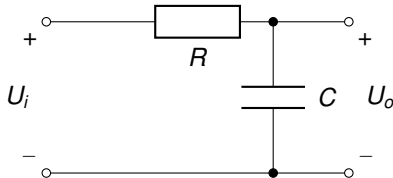



- ▶ Example: First order low-pass

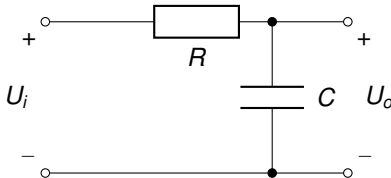


- ▶ Complex voltage divider

$$U_o = U_i \left| \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right| = U_i \left| \frac{1}{1 + j\omega CR} \right| = U_i \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

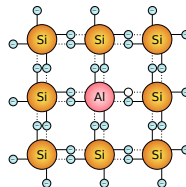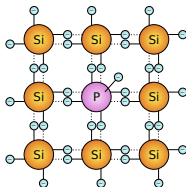- ▶ Silicon, Germanium, ...
- ▶ Strong covalent bonding
 - ▶ No free movable charge for current flow
- ▶ Electric conductivity increases with
 - ▶ Temperature
 - ▶ n-type doping with donator
 - ▶ p-type doping with acceptor



► PN junction

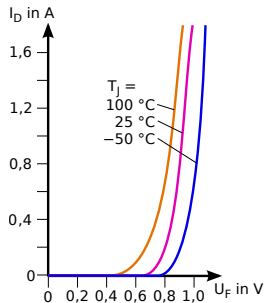


► MULTICOMP 703-0090

- Forward voltage 1.8 V
- Operating current 20 mA
- Reverse voltage -4 V

► Required series resistor for $U = 5\text{ V}$



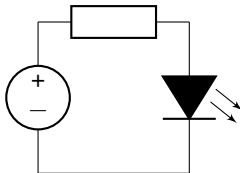
$$R = \frac{U_R}{I_D} = \frac{U - U_D}{I_D} = 160\ \Omega$$



Bipolar-Junction-Transistor




TECHNISCHE
UNIVERSITÄT
DARMSTADT

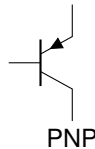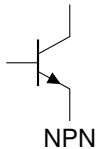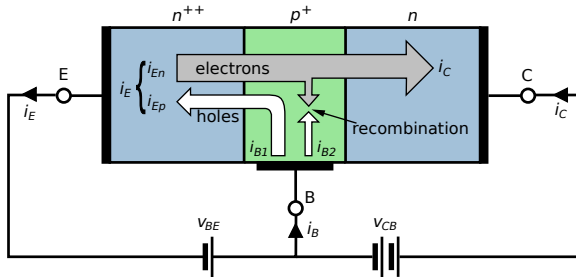

MOSFET



TECHNISCHE
UNIVERSITÄT
DARMSTADT

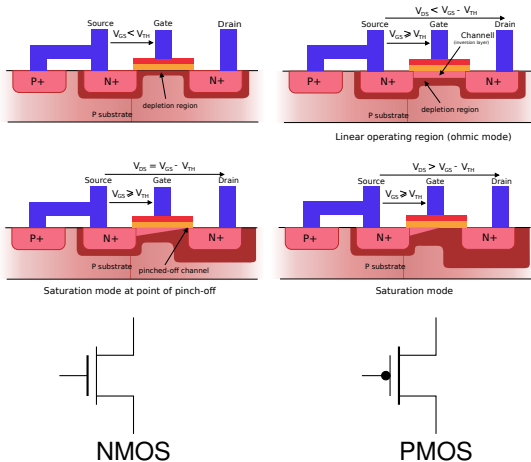

Embedded Systems Hands-On 1: Design and Implementation of Hardware/Software Systems

{heinz,hofmann}@esa.tu-darmstadt.de



TECHNISCHE
UNIVERSITÄT
DARMSTADT

